

Experiment No. 5  
Frequency Response of Active Networks  
ECE 213

Peter CHINETTI

October 29, 2013

Date Performed: October 23, 2013  
Instructor: Professor Shanechi

## 1 Introduction

Filters are often used to modify and process analog signals. Filters are needed in electronic systems to amplify certain frequency components of a composite signal and to attenuate other frequency components. This lab had the experimenters build two types of active filters: the Butterworth and the Chebyshev.

## 2 Background

A second order voltage transfer function for a low-pass filter can be expressed as:

$$\frac{V_2(s)}{V_1(s)} = \frac{H_0\omega_n^2}{s^2 + s\frac{\omega_n}{Q} + \omega_n^2} \quad (1)$$

When implementing this transfer function in hardware, an op-amp in non-inverting configuration is paired with external resistors and capacitors. Figure 1 is the diagram for the non-inverting amplifier, figure 2 is the external circuit. In figure 2, the op-amp with its input tied together is a stand in for the non-inverting amplifier circuit. In figures 3 and 4, the values for all components are listed.

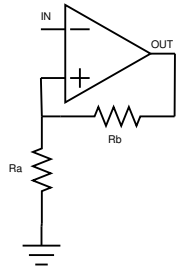


Figure 1: Non-inverting amplifier

$\omega_n$	5287
Q	1.306
R	20 k $\Omega$
C	9.4 nF
Gain	2.2243
$R_b$	240 $\Omega$
$R_a$	200 $\Omega$

Figure 3: Chebyshev Filter

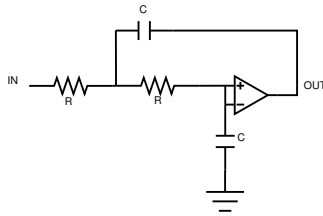


Figure 2: Second order filter

$\omega_n$	6283
Q	0.707
R	15 k $\Omega$
C	10 nF
Gain	1.585
$R_b$	240 $\Omega$
$R_a$	470 $\Omega$

Figure 4: Butterworth Filter

### 3 Procedure


- a. Calculate resistance and capacitance values for each circuit.
- b. Build circuits.
- c. Set function generator to sweep output, with logarithmic sweep rate.
- d. Set scope to a slow sweep rate.
- e. Time single sweep with scope with sweep out of function generator.

### 4 Equipment


- Oscilloscope
- Function generator
- Resistors
- Capacitors

### 5 Data and Graphs


#### 5.1 Input Function

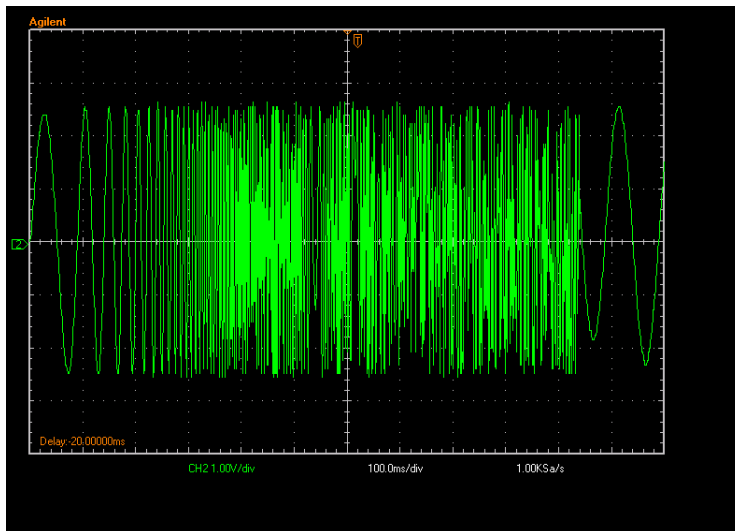

## 5.2 Chebyshev Filter

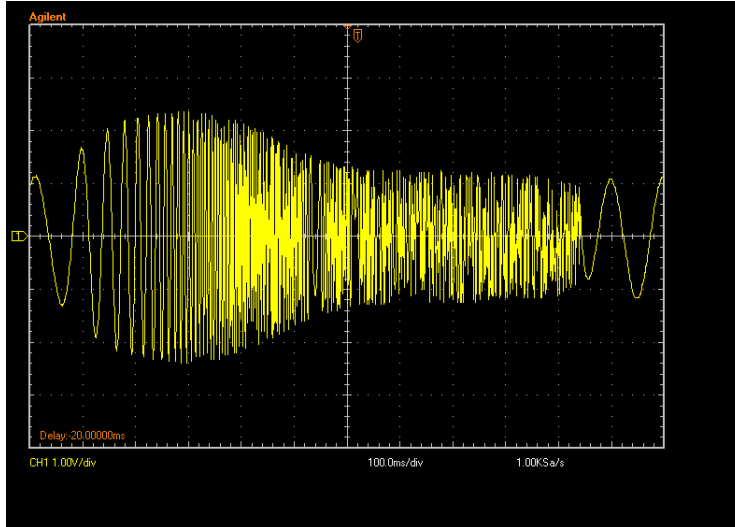

## 5.3 Butterworth Filter

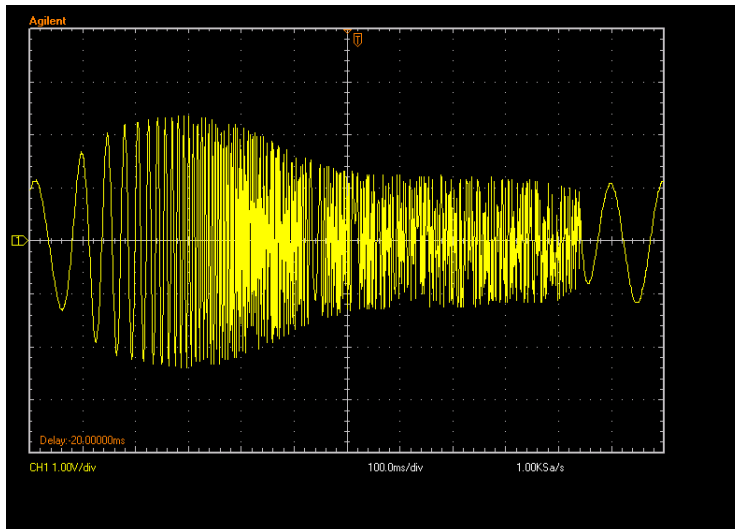

## 6 Conclusions

The purpose of this lab was achieved. A Butterworth and a Chebyshev filter with a 1kHz cutoff were built and tested. Both filters seemed to have very similar responses.