

Experiment No. 6  
Transformer Principles  
ECE 213

Peter CHINETTI

November 3, 2013

Date Performed: October 30, 2013  
Instructor: Professor Shanechi

## 1 Introduction

A mutual inductance can be used to model two inductors which share a common magnetic path. This combination is a 'transformer'. Transformers are frequently used to convert a higher voltage to a lower voltage, such as in the power supplies of computers, or on the utility pole near houses. Transformers can also be used to convert a lower voltage to a higher voltage, such as in the electron gun in CRT monitors.

## 2 Background

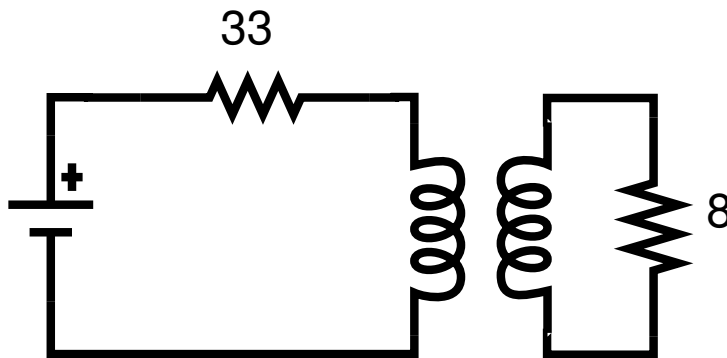


Figure 1: Lab Circuit

In the circuit in Figure 1, the resistance of from across the transformer is reflected back to the primary side according to the equation:

$$Z_{in} = \frac{Z_l}{n^2} \quad (1)$$

Therefore, the reflected impedance is  $32\Omega$  (Power across the the reflected impedance is .121 Watts). This is quite different than simply moving the  $8\Omega$  (Power across the series impedance is .076 Watts),  $32\Omega$  is much closer to the ideal resistance to transfer power to the  $8\Omega$  resistor.

### 3 Procedure

- a. Calculate expected power
- b. Build circuits
- c. Test circuit

### 4 Equipment

- Oscilloscope
- Function generator

### 5 Data

Graphs of the measured voltages can be found in Figures 3-5. In these graphs, green is the input voltage, yellow is the output voltage (typically measured across the  $8\Omega$ ). A table of measured  $V_{pp}$  values can be found in the table of Figure 6.

### 6 Conclusions

The purpose of this lab was achieved. A circuit was built with and a transformer to perform impedance matching. The measured power dissipated by the resistor close to doubled when the transformer was introduced.

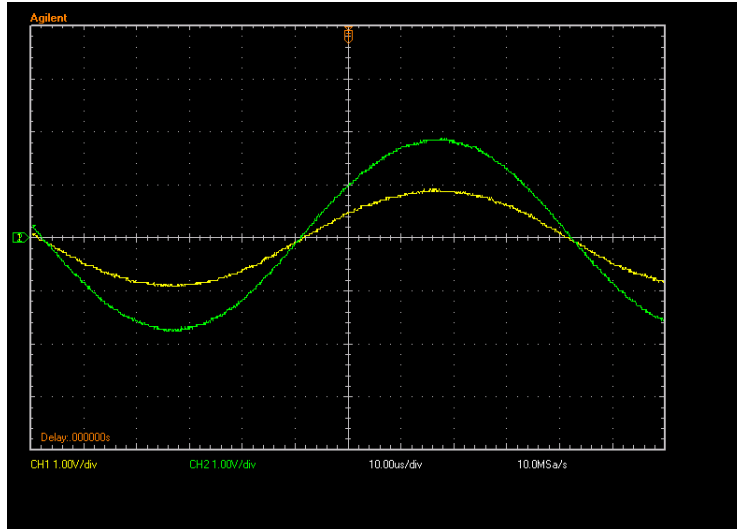


Figure 2: Unloaded Transformer

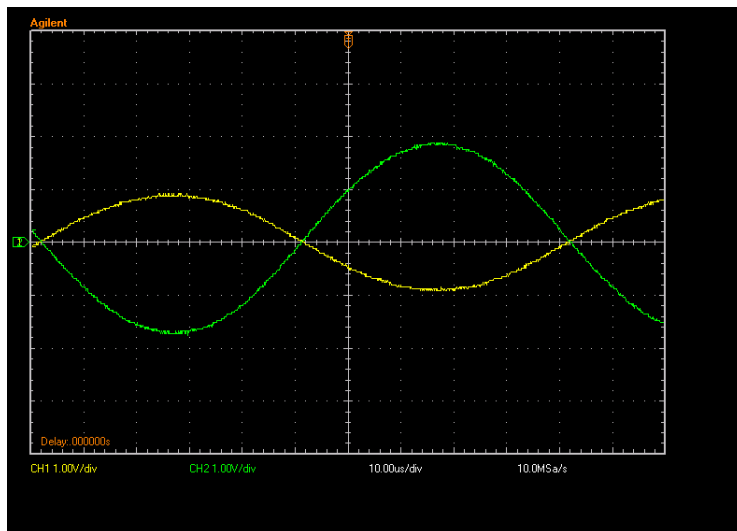


Figure 3: Unloaded Transformer With Flipped Outputs

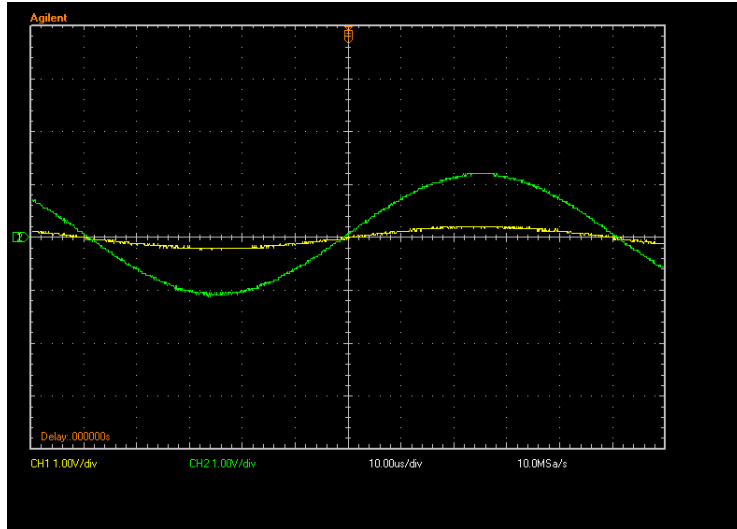


Figure 4: Voltage Divider

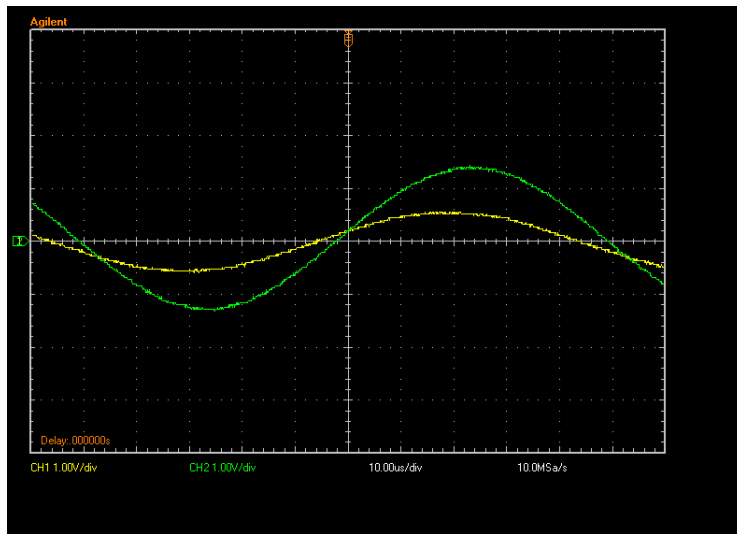


Figure 5: Reflected

Circuit	Input Voltage	Output Voltage	Power Dissipated in $8\Omega$ Resistor
Unloaded	3.641	1.841	
Divider	3.261	.440	.0242
Transformer	2.721	.6	.045

Figure 6:  $V_{pp}$  Values