

Sequential Circuits

I. INTRODUCTION :

The output of a combinational circuit depends only on the inputs of circuits. This means combinational circuits do not have any memory elements. Sometimes a circuit's next value depends on its past value. This means we need to store the previous value to figure out the next value. For example, a sequence detector for 100 needs to have previous information stored. In this section, Clocked Synchronous State Machine analysis will be done. There are two different FSMs(finite state machines):

- Moore Machine: If output is only function of a state
- Mealy Machine: If output is function of state and inputs.

 


Figure 1 : Moore Machine

 


Figure 2 : Mealy Machine

II. BASIC ELEMENTS :

D-Flip flop

One of the main elements in FSM design is D-FF. State memories shown in Figures 1 and 2 can be designed using D-FF or other memory elements such as J-K Flip flops, T-Flip flops, and so on. In this section, the design would be done using D-FF but you may need to use other memory elements as well. D Flip Flops can be designed as follows:

- D-FF (Input D will be transferred to output Q when Clk is positive edge. At all other times the previous value will be held)

 


Figure 3.a : D-FF with Positive edge Clk

Clk	D	Q
\uparrow	D	D
0	D	Q_0
1	D	Q_0

Figure 3.b : D-FF with Positive edge Clk Truth Table

VHDL Code and Simulation:

```
library ieee;
use ieee.std_logic_1164.all;
entity DFF is
    port(
        D : in std_logic;
        Clk : in std_logic;
        Q : out std_logic);
end DFF;

architecture behavior of DFF is
begin
    process (Clk)
    begin
        if (Clk'event and Clk='1') then
            Q <= D;
        end if;
    end process;
end behavior;
```

TestBench

```
library ieee;
use ieee.std_logic_1164.all;

entity DFF_Test is
end DFF_Test;

architecture behavior_test of DFF_Test is
    constant T: time := 100 ns;
    signal D_Test : std_logic;
    signal Clk : std_logic;
    signal Q_Test : std_logic;

begin
    DUT: entity work.DFF
        port map (D => D_Test, Clk => Clk, Q => Q_Test);

    process
    begin
        Clk <= '0';
        wait for T/2;
        Clk <= '1';
        wait for T/2;
    end process;

    process
    begin
        D_Test <= '0';
        wait for 2*T;
        D_Test <= '1';
        wait for 3*T;
        D_Test <= '0';
    end process;

end behavior_test;
```

 


Figure 4 : Simulation Results

- D-FF with Asynchronous Reset (Input D will be transferred to output Q when Clk is positive edge. At all other times, the previous value will be held. Reset can reset the Q to zero at any time independently from Clk)

 


Figure 5.a : D-FF with Asynchronous Reset

Clk	D	Reset	Q
---	---	0	0
	D	1	D
0	D	1	Q ₀
1	D	1	Q ₀

Figure 5.b : Truth Table

VHDL Code and Simulation:

```
library ieee;
use ieee.std_logic_1164.all;
entity DFF_Reset is
    port(
        D : in std_logic;
        Clk : in std_logic;
        Reset : in std_logic;
        Q : out std_logic);
end DFF_Reset;
```

```
architecture behavior of DFF_Reset is
begin
    process (Clk,Reset)
    begin
        if (Reset = '0') then
            Q <= '0';
        elsif (Clk'event and Clk='1') then
            Q <= D;
        end if;
    end process;
end behavior;
```

-- Change of Clk and Reset .

-- Clk event and positive edge. (Change Clk='0' for negative edge)

TestBench

```
library ieee;
use ieee.std_logic_1164.all;
```

```
entity DFF_Reset_Test is
end DFF_Reset_Test;
```

```
architecture behavior_test of DFF_Reset_Test is
    constant T : time := 100 ns;
    signal D_Test : std_logic;
    signal Clk : std_logic;
    signal Reset_Test : std_logic;
    signal Q_Test : std_logic;
begin
```

-- Constant for clock period

-- Inputs and outputs are declared as signals

```
DUT: entity work.DFF_Reset
port map (D => D_Test, Clk => Clk, Reset => Reset_Test, Q => Q_Test);
```

-- Instantiation of Design Under Test

```
process
```

```

begin
    Clk <= '0';
    wait for T/2;
    Clk <= '1';
    wait for T/2;
end process;

process
begin
    Reset_Test <= '0';
    D_Test <= '0';
    wait for 2*T;
    D_Test <= '1';
    wait for T;
    Reset_Test <= '1';
    wait for 2*T;
    D_Test <= '0';
    wait for 3*T;
    D_Test <= '1';
end process;

end behavior_test;

```


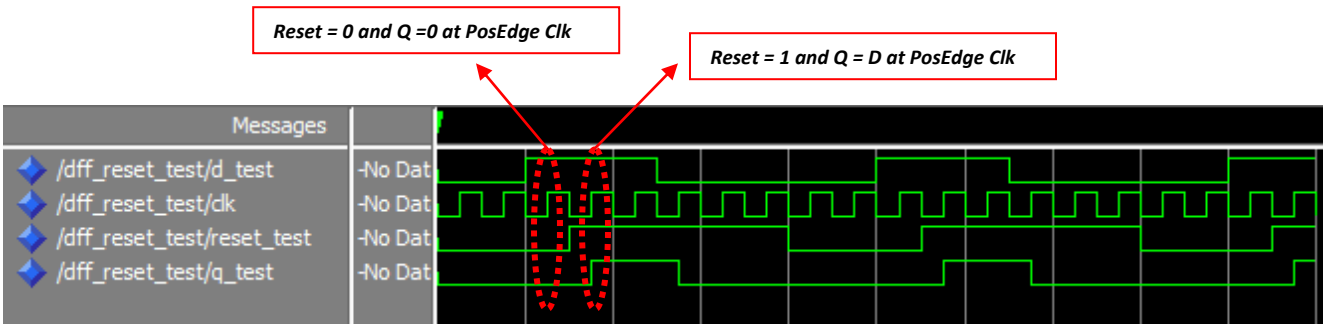


Figure 6 : Simulation Results

 - D-FF with Asynchronous Reset and Synchronous Enable (Input D will be transferred to output Q when Clk is positive edge. At all other times, the previous value will be held. Reset can reset the Q to zero at any time independently from Clk and D-FF will be enabled when E=1 is at positive Clk edge).



Clk	D	E	Reset	Q
---	---	---	0	0
↑	D	1	1	D
↑	D	0	1	Q ₀
0	D	---	1	Q ₀
1	D	---	1	Q ₀

Figure 7.a : D-FF with Asynchronous Reset

Figure 7.b : Truth Table

VHDL Code and Simulation:

```

library ieee;
use ieee.std_logic_1164.all;
entity DFF_R_E is
port(
    D : in std_logic;
    Clk : in std_logic;

```

```

Reset : in std_logic;
Enable: in std_logic;
Q : out std_logic);
end DFF_R_E;

```

architecture behavior of DFF_R_E is

```

begin
  process (Clk,Reset)
  begin
    if (Reset = '0') then
      Q <= '0';
    elsif (Clk'event and Clk='1') then
      if (Enable = '1') then
        Q <= D;
      end if;
    end if;
  end process;
end behavior;

```

-- Change of Clk and Reset (Enable is not is process).

-- Clk event and positive edge. (Change Clk='0' for negative edge)

-- During posedge clock whenever Enable = 1 , Q = D

-- During posedge clock whenever Enable =0 , Q = Q₀

TestBench

```

library ieee;
use ieee.std_logic_1164.all;

```

```

entity DFF_R_E_Test is
end DFF_R_E_Test;

```

architecture behavior_test of DFF_R_E_Test is

```

constant T: time := 100 ns;
signal D_Test : std_logic;
signal Clk : std_logic;
signal Reset_Test : std_logic;
signal Enable_Test : std_logic;
signal Q_Test : std_logic;
begin

```

-- Constant for clock period

-- Inputs and outputs are declared as signals

DUT: entity work.DFF_R_E

```

port map (D => D_Test, Clk => Clk, Reset => Reset_Test, Enable => Enable_Test, Q => Q_Test);

```

```

process
begin
  Clk <= '0';
  wait for T/2;
  Clk <= '1';
  wait for T/2;
end process;

```

-- Constant for clock period

```

process
begin
  Reset_Test <= '0';
  D_Test <= '0';
  Enable_Test <= '0';
  wait for 2*T;
  D_Test <= '1';
  wait for T;
  Reset_Test <= '1';
  wait for 2*T;
  D_Test <= '0';
  wait for 3*T;
  D_Test <= '1';
  Enable_Test <= '1';
  wait for 2*T;
  D_Test <= '0';
  wait for 2*T;
  D_Test <= '1';
  wait for 6*T;

```

-- Clock that runs T=100 ns

-- Generation of input vectors.

end process;

end behavior_test;

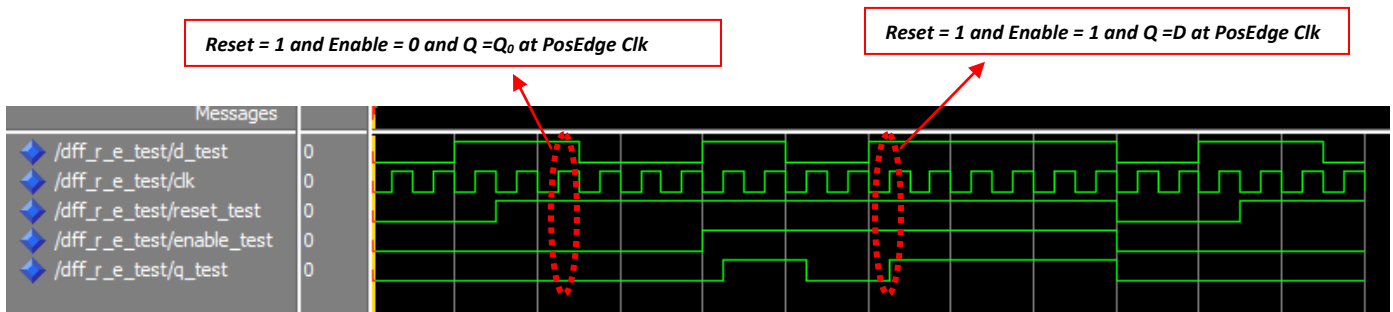


Figure 8 : Simulation Results

Finite State Machine (FSM)

A state machine is specified by State Diagrams. As described in the beginning, FSM can be a Moore or Mealy machine. A state diagram is made of nodes with a transition arrow between the nodes. Nodes represent states and transition arrows represent logic expressions. The arrow direction represents the transaction from current state to the next state and this will happen when the transaction arrow logic expression is true. Figures 9.1 and 9.2 show node and transaction arrows of Mealy and Moore machines, respectively.

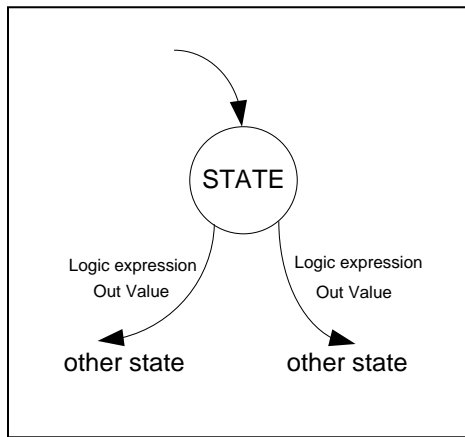


Figure 9.1 : Mealy Machine

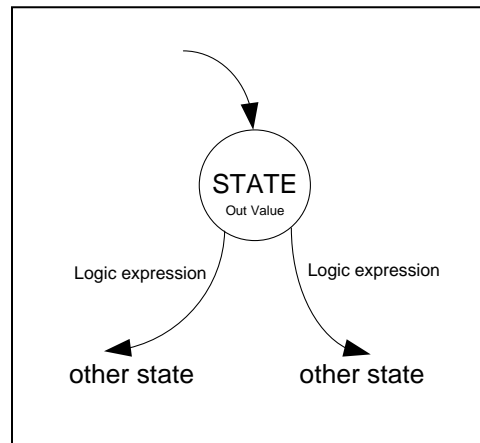


Figure 9.2 : Moore Machine

Device Type	Characteristic Equation
S-R Latch	$Q^* = S + R'.Q$
D Latch	$Q^* = D$
Edge-triggered D flip-flop	$Q^* = D$
D flip-flop with Enable	$Q^* = EN.D + EN'.Q$
Master/slave S-R flip-flop	$Q^* = S + R'.Q$
Master/slave J-K flip-flop	$Q^* = J.Q' + K'.Q$
Edge Triggered J-K flip-flop	$Q^* = J.Q' + K'.Q$
T flip-flop	$Q^* = Q'$
T flip-flop with enable	$Q^* = EN.Q' + EN'.Q$

Figure 10. Latch and flip-flop characteristic equations

State Machine VHDL Code:

Mealy Machine: We mostly use 2 processes

- Modeling the state registers and decide the next state
- Updating the output and next state

Moore Machine: We mostly use 2-3 processes

- Modeling the state registers and decide the next state
- Updating the next state
- Output logic

VHDL CODE EXAMPLE

In this section, we will examine a simple state diagram and its VHDL code. Please check the comments carefully.

a. Moore Machine:

 


Figure 10.1 : State Diagram

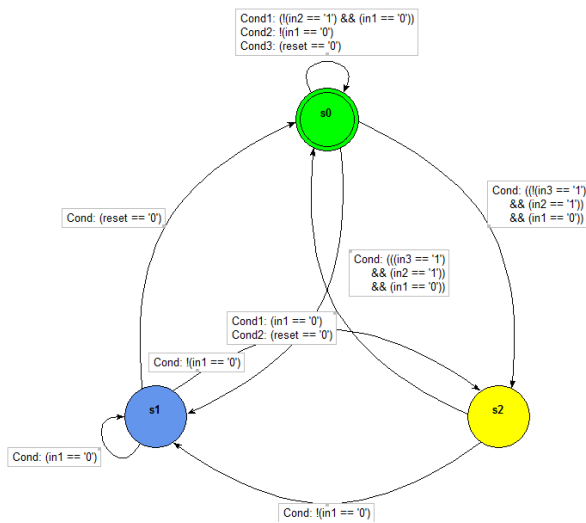


Figure 10.2 : State Diagram (Generated via Modelsim)

```

library ieee;
use ieee.std_logic_1164.all;
entity FSM_MOORE is
  port(
    Reset : in std_logic;
    In1, In2, In3 : in std_logic;
    Clk : in std_logic;
    Out1 : out std_logic);
end FSM_MOORE;

```

```

architecture behavior of FSM_MOORE is
  type states is (S0, S1, S2);
  signal present_state, next_state : states;
begin
  process (Clk, Reset)
  begin
    if (Reset = '0') then
      present_state <= S0;
    elsif (Clk'event and Clk='1') then
      present_state <= next_state;
    end if;
  end process;

```

```

  process (present_state, In1, In2, In3)
  begin
    case present_state is
      when S0 =>
        if In1 = '0' then
          if In2='1' then
            if In3='1' then
              next_state <= S1;
            else
              next_state <= S2;
            end if;
          else
            next_state <= S0;
          end if;
        else
          next_state <= S0;
        end if;
      when S1 =>
        if In1 = '0' then
          next_state <= S1;
        else
          next_state <= S2;
        end if;

```

- User defined enumerator "states"
- Using enumerator "states" as signal
- Clk and Reset in process (Asynchronous Reset).
- When Reset = 0 State = S0
- When Reset = 1 and posedge Clk state assignment
- present_state, and inputs are in process
- Transition to S1 when (~In1 & In2 & In3)
- Transition to S2 when (~In1 & In2 & ~In3)
- Transition to S0 all others
- When State is S1 stay at S1 when (In1)
- When State is S1 transition to S2 when (~In1)

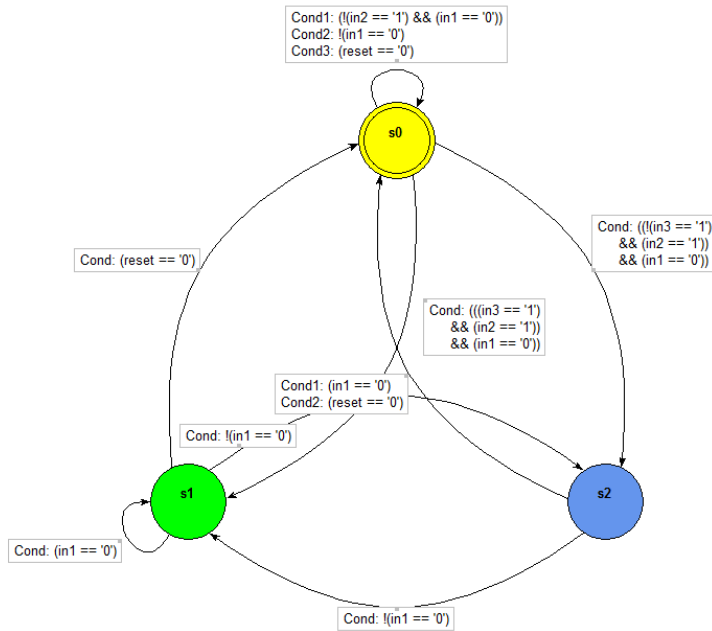


Figure 12.2 : State Diagram (Generated via Modelsim)

```

library ieee;
use ieee.std_logic_1164.all;
entity FSM_MEALY is
    port(
        Reset : in std_logic;
        In1, In2, In3 : in std_logic;
        Clk : in std_logic;
        Out1 : out std_logic);
end FSM_MEALY;
  
```

```

architecture behavior of FSM_MEALY is
    type states is (S0, S1, S2);
    signal present_state, next_state : states;
begin
    process (Clk, Reset)
    begin
        if (Reset = '0') then
            present_state <= S0;
        elsif (Clk'event and Clk='1') then
            present_state <= next_state;
        end if;
    end process;
  
```

```

-- User defined enumerator "states"
-- Using enumerator "states" as signal
-- Clk and Reset in process ( Asynchronous Reset).
-- When Reset = 0 State = S0
-- When Reset = 1 and posedge Clk state assignment
  
```

```

process (present_state, In1, In2, In3)
begin
    case present_state is
        when S0 =>
            if In1 = '0' then
                if In2='1' then
                    if In3='1' then
                        next_state <= S1;
                    else
                        next_state <= S2;
                    end if;
                else
                    next_state <= S0;
                end if;
            else
                next_state <= S0;
            end if;
        end if;
    end case;
  
```

```

-- present_state, and inputs are in process
-- Transition to S1 when (~In1 &In2&In3)
-- Transition to S2 when (~In1 &In2&~In3)
-- Stay at S0 all others
  
```

```

when S1 =>
  if In1 = '0' then
    next_state <= S1;
  else
    next_state <= S2;
  end if;

when S2 =>
  if In1 = '0' then
    next_state <= S0;
  else
    next_state <= S1;
  end if;
end case;
end process;

process (present_state, In1, In2, In3)
begin
  case present_state is
    when S0 =>
      if (In1 = '0' and In2 = '1' and In3 = '1') then
        Out1 <= '0';
      else
        Out1 <= '1';
      end if;
    when S1 =>
      if In1 = '0' then
        Out1 <= '0';
      else
        Out1 <= '1';
      end if;
    when S2 =>
      Out1 <= '0';
  end case;
end process;

end behavior;

```

-- When State is S1 stay at S1 when (In1)
-- When State is S1 transition to S2 when (~In1)

-- When State is S2 transition to S0 when (~In1)
-- When State is S2 transition to S1 when (In1)

-- Mealy machine process for output.(present_state and inputs are in process)

-- Output depends on state values and inputs. This could have integrated
-- into previous process.

 


Figure 13 : Simulation Results

DESIGN EXAMPLE (SEQUENCE RECOGNIZER for “101”):

